

# Circuits and Transforms

Himanshu Kumar Gupta

## CONTENTS

**Abstract**—This manual provides a simple introduction to Transforms

### 1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of  $g(t)$  is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

### 2 LAPLACE TRANSFORM

1. In the circuit, the switch  $S$  is connected to position  $P$  for a long time so that the charge on the capacitor becomes  $q_1 \mu C$ . Then  $S$  is switched to position  $Q$ . After a long time, the charge on the capacitor is  $q_2 \mu C$ .


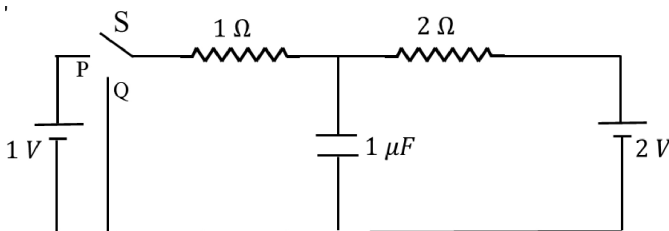


Fig. 2.1


2. Draw the circuit using latex-tikz.

**Solution:**

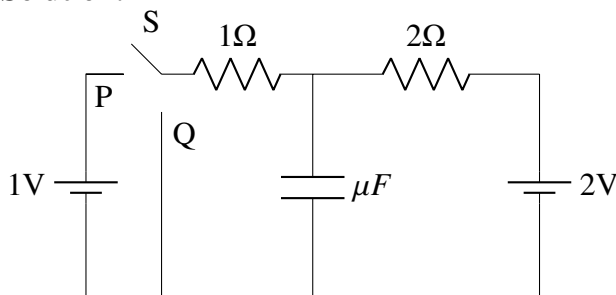

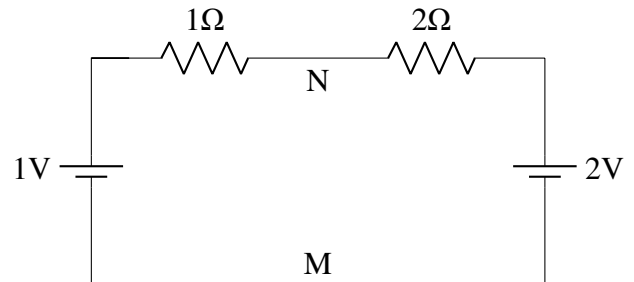3. Find  $q_1$ .

**Solution:** On connecting  $S$  to  $P$  for a long time make the capacitor fully charged. So, it will behave like disconnected wire. So, circuit will look like



So, on applying KVL we get current as,

$$i = 1/3 \quad (2.1)$$

in counter-clockwise direction

So, PD across the capacitor i.e. between  $M$  and  $N$  is given by,

$$V_Q = 1 + \frac{1}{3} \times 1 \quad (2.2)$$

$$= \frac{4}{3} \quad (2.3)$$

Now, charge on capacitor will be

$$q_1 = V_Q C_0 \quad (2.4)$$

$$= \frac{4}{3} \mu C \quad (2.5)$$

4. Show that the Laplace transform of  $u(t)$  is  $\frac{1}{s}$  and find the ROC.

**Solution:** Laplace of  $u(t)$  is given by

$$U(t) = \int_{-\infty}^{\infty} u(t)e^{-st} dt \quad (2.6)$$

$$= \int_0^{\infty} e^{-st} dt \quad (2.7)$$

$$= \left[ \frac{e^{-st}}{-s} \right]_0^{\infty} \quad (2.8)$$

$$= \frac{1}{s} \quad (2.9)$$

Since  $e^{-st}$  is defined at  $t \rightarrow \infty$  only for  $s_0 > 0$

So, ROC will be  $s > 0$

5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{H}} L \frac{1}{s+a}, \quad a > 0 \quad (2.10)$$

and find the ROC.

**Solution:**

$$\mathcal{L}[e^{-at}u(t)] = \int_{-\infty}^{\infty} e^{-at}u(t)e^{-st} dt \quad (2.11)$$

$$= \int_{-\infty}^{\infty} e^{-at}u(t)e^{-st} dt \quad (2.12)$$

$$= \int_0^{\infty} e^{-(a+s)t} dt \quad (2.13)$$

$$= \left. \frac{e^{-(s+a)t}}{-(s+a)} \right|_0^{\infty} \quad (2.14)$$

$$= \frac{1}{s+a} \quad (2.15)$$

Since  $e^{-(s+a)t}$  is defined at  $t \rightarrow \infty$  only for  $s < -a$

So, ROC will be  $s > -a$

6. Now consider the following resistive circuit transformed from Fig. ?? where

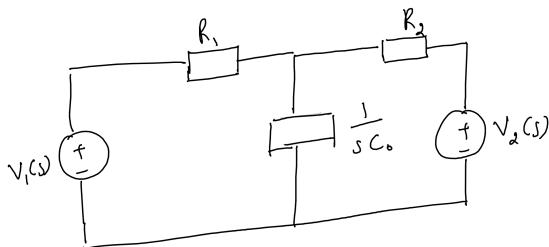


Fig. 2.2: hbhb

$$u(t) \xleftrightarrow{\mathcal{H}} LV_1(s) \quad (2.16)$$

$$2u(t) \xleftrightarrow{\mathcal{H}} LV_2(s) \quad (2.17)$$

Find the voltage across the capacitor  $V_{C_0}(s)$ .

**Solution:** Given that  $V_1(s) = \frac{1}{s}$  and  $V_2(s) = \frac{2}{s}$

7. Find  $v_{C_0}(t)$ . Plot using python.
8. Verify your result using ngspice.
9. Obtain Fig. ?? using the equivalent differential equation.

$R_1, R_2, C_0$  for the passive elements. Use latex-tikz.

3.  $V_{C_0}(s) = ?$
4.  $v_{C_0}(t) = ?$  Plot using python.
5. Verify your result using ngspice.
6. Find  $v_{C_0}(0-), v_{C_0}(0+)$  and  $v_{C_0}(\infty)$ .
7. Obtain the Fig. in problem ?? using the equivalent differential equation.

#### 4 BILINEAR TRANSFORM

1. In Fig. ??, consider the case when  $S$  is switched to  $Q$  right in the beginning. Formulate the differential equation.
2. Find  $H(s)$  considering the output voltage at the capacitor.
3. Plot  $H(s)$ . What kind of filter is it?
4. Using trapezoidal rule for integration, formulate the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (4.1)$$

5. Find  $H(z)$ .
6. How can you obtain  $H(z)$  from  $H(s)$ ?

#### 3 INITIAL CONDITIONS

1. Find  $q_2$  in Fig. ??.
2. Draw the equivalent  $s$ -domain resistive circuit when  $S$  is switched to position  $Q$ . Use variables